

### P3 - ELT 225 - Mag 2

Name: Weritson Frederico da C. Alves Matricula: 96708 Data: 9/12/20

$$\textcircled{1} \quad d = 0, V_0 = 100 \angle 0^\circ \text{ V}, R_g = 25 \Omega, f = 100 \text{ MHz}, L_1 = 2 \text{ m}, \epsilon_{n_1} = 2.25$$

$$Z_{01} = 50 \Omega, Z_{L1} = 50 + j50, L_2 = 1 \text{ m}, Z_{02} = 75 \Omega, Z_{L2} = 50 + j10 \Omega, \epsilon_{n_2} = 2.25,$$

$$\underline{\epsilon_{n_3} = 4, Z_{03} = 100 \Omega, L_3 = 2 \text{ m}, Z_{L3} = 100 - j50 \Omega}$$

$$\textcircled{2} \quad \left. \begin{aligned} Z_{L2} &= \frac{Z_{L2}}{Z_{02}} = \frac{50 + j10}{75} = 0.667 + 0.133j \\ Z_{L3} &= \frac{Z_{L3}}{Z_{03}} = \frac{100 - j50}{100} = 1 - 0.5j \end{aligned} \right\} \begin{aligned} B_2 &= \frac{2\pi f}{\sqrt{\epsilon_0 \mu_0}} = 2\pi f \sqrt{\epsilon_0 \mu_0} \cdot 2.25 = 3.144 = B_1 \\ B_3 &= 2\pi f \sqrt{4 \mu_0 \epsilon_0} = 4.192 \\ B_1 L_2 &= 6.288 \\ B_3 L_3 &= 8.384 \end{aligned}$$

$$Z_{in_2} = 75 \left[ \frac{(50 + j10) + j \frac{1}{2}(3.144)}{75 + j(50 + j10) \frac{1}{2}(3.144)} \right] = 51.016 + 10.077j \quad \left. \begin{aligned} \lambda_1 &= \frac{2\pi}{B_1} = 1.998 \text{ m} \\ \lambda_3 &= \frac{2\pi}{B_3} = 1.499 \text{ m} \end{aligned} \right\}$$

$$Z_{in_3} = 100 \left[ \frac{(100 - j50) + j \frac{1}{2}(6.288)}{100 + j(100 - j50) \frac{1}{2}(6.288)} \right] = 133.348 + 47.134j$$

$$\left. \begin{aligned} \lambda_1 &= 1.998 \text{ m} \\ \lambda_1' &= 2 \text{ m} \end{aligned} \right\} \lambda' = 1.001\lambda \quad \left. \begin{aligned} \lambda_2 &= 1.998 \text{ m} \\ \lambda_2' &= 1 \text{ m} \end{aligned} \right\} \lambda_2' = 0.501\lambda \quad \left. \begin{aligned} \lambda_3 &= 1.499 \text{ m} \\ \lambda_3' &= 2 \end{aligned} \right\} \lambda_3' = 1.334\lambda$$

$$Z_{eq} = Z_{in_3} // Z_{in_2} = 37.063 + 8.83j \rightarrow Z_{eq} = Z_{L1} + Z_g = 86.53 + j58.83$$

$$Z_{in_1} = 50 \left[ \frac{Z_{eq} + j50 \frac{1}{2}(3.144)}{50 + jZ_{eq} \frac{1}{2}(3.144)} \right] = 87.89 + j59.89$$

$$I_0 = \frac{100 \angle 0^\circ}{25 + Z_{in_1}} = 0.691 - 0.367j = 0.783 \angle -0.488 \text{ rad}$$

$$V_1 = 55.7654 \quad V_2 = V_3 = 29.62 \text{ V}$$

$$P_{Z_{L1}} = \frac{55.76^2}{2 \cdot 50} = 31.5 \text{ W} \quad \left. \begin{aligned} P_2 &= \frac{29.62}{2 \times 51} = 8.601 \text{ W} \\ P_3 &= \frac{29.62}{133.3 \times 2} = 3.29 \text{ W} \end{aligned} \right\}$$

$$b) S = \frac{1 + T_c^r}{1 - T_c^r} = 2.62$$

$$i) T_c^r = \frac{50 + j50 - 50}{50 + j50 + 50} = 0.45 \angle 63.43^\circ$$

$$ii) T_c^r = \frac{50 + j10 - 75}{50 + j10 + 75} = 0.215 \angle 153.6^\circ$$

$$S = -1.55$$

$$iii) T_c^r = \frac{100 - j50 - 100}{100 - j50 + 100} = 0.24 \angle -75.56^\circ$$

$$S = 1.64$$

c)  $\frac{50 + j10}{j5} = 0.6667 + j0.1383$ , logo temos que os máximos  
serão em  $0.25\lambda - 0.02\lambda = 0.23\lambda$  e os mínimos em  $0.02\lambda$

$$d) 2.6686 \rightarrow \left. \begin{array}{l} \text{02 máximas} \\ \text{03 mínimas} \end{array} \right\} \underline{Z} = (6.6667 - j2.362) \times 10^{-3}$$

②  $S = 3:1$ ,  $V_{max} 0,5\lambda$

$$z_L = 3 + j0 \text{ em } 0,25\lambda, V_L = 0,333 + j0 \text{ em } 0\lambda$$

Ponto de encontro do círculo S com o círculo  $n=1$ :  $1 + j1,15j$

$$0,167\lambda - j0\lambda = \underline{0,167\lambda}$$

Logo o comprimento da estrada é:

$$1 - j1,15 \rightarrow 0,333\lambda$$

$$d = 0,5\lambda - 0,333\lambda = 0,167\lambda$$

$$\textcircled{3} \quad \alpha = 0, Z_0 = 75 \Omega, L = 20 \text{ m}, f = 32 \times 10^6 \text{ Hz}, Z_{in} = 30 \Omega$$

$$\text{a)} \quad Z_{in} = Z_0 \left[ \frac{Z_L + j Z_0 \operatorname{tg}(BL)}{Z_0 + j Z_L \operatorname{tg}(BL)} \right] \Rightarrow 30 = 75 \cdot \left[ \frac{Z_L + j 75 \operatorname{tg}(13.41)}{75 + j Z_L \operatorname{tg}(13.41)} \right] = *$$

$$\beta = \frac{\omega}{V_p} \Rightarrow \frac{2\pi f}{\sqrt{\mu_0 \epsilon_0}} = 0.67 \Rightarrow \boxed{BL = 13.41} \quad \left. \begin{array}{l} * \Rightarrow Z_L = 55.96 - j58.44 \\ \approx 56 - j58 \Omega \end{array} \right\}$$

$$Z_L = 0.75 - 0.78j$$

$$\text{b)} \quad Z_{in} = 75 + j X_{in}, \quad X_{in} > 0 \quad \text{e} \quad X_{in} = ?$$

$$\boxed{Z_{in} = 1 + j \frac{X_{in}}{75}} \quad \text{i) Ver onde os círculos se cruzam os círculos } \Pi = 1 \text{, quando } X_{in} > 0.$$

ii) Pela carta de Smith, temos:

$$Z_{in}' = 1 + 0.95j \Rightarrow 0.16\lambda \quad (X_{in} > 0)$$

$$Z_{in}'' = 1 - 0.95j \Rightarrow 0.34\lambda \quad (X_{in} < 0)$$

$$Z_L \approx 0.367\lambda \quad \left\{ d = 0.207\lambda \Rightarrow D = 1.941 \text{ m} \right.$$

$$X_{in} = Z_0 \cdot Z_{in} = \underline{75.2552} \quad \checkmark$$

$$\lambda = \frac{V_p}{f} = \frac{c}{f} = 9.375 \text{ m}$$

④

$$I_{\min} - I_{\max} = \frac{\lambda}{4} = 37,5 \text{ cm} - 12,5 \text{ cm} = 25 \text{ cm} \Rightarrow \lambda = 1 \text{ m}$$

$$V = f \cdot \lambda \Rightarrow f = \frac{3 \cdot 10^8}{1} = 310^8 \text{ Hz} \quad \left\{ \begin{array}{l} 0,5 - 360 \\ 0,125 - x \\ x = 90^\circ \\ \text{na direção da gerador} \end{array} \right.$$

$$Z = Z_0, Z_1$$

$$= (0,38 + 0,93j) 100$$

$$= \underline{38 + 93j} \quad \checkmark$$

$$⑤ H(z, t) = 2 \cos(\omega t - \beta z) \hat{a}_x + 6 \cos(\omega t - \beta z + 120^\circ) \hat{a}_y \text{ A/m}$$

$$A = (0, 0) = 2 \hat{a}_x + 6 \cos(120^\circ) \hat{a}_y = 2 \hat{a}_x - 3 \hat{a}_y$$

$$B = \left(0, \frac{T}{4}\right) = 2 \cos\left(\frac{\pi}{2}\right) \hat{a}_x + 6 \cos\left(\frac{\pi}{2} + 120^\circ\right) \hat{a}_y = 0 \hat{a}_x - 3\sqrt{3} \hat{a}_y$$

$$C = \left(0, \frac{T}{2}\right) = 2 \cos(\pi) \hat{a}_x + 6 \cos(\pi + 120^\circ) \hat{a}_y = -2 \hat{a}_x + 3 \hat{a}_y$$

$$D = \left(0, \frac{3T}{4}\right) = 2 \cos\left(\frac{3\pi}{2}\right) \hat{a}_x + 6 \cos\left(\frac{3\pi}{2} + 120^\circ\right) \hat{a}_y = 0 \hat{a}_x + 3\sqrt{3} \hat{a}_y$$

$$E = (0, T) = 2 \cos(2\pi) \hat{a}_x + 6 \cos(2\pi + 120^\circ) \hat{a}_y = 2 \hat{a}_x - 3 \hat{a}_y$$

$$\left. \begin{aligned} T &= \frac{1}{f} \quad \omega = 2\pi f \\ \omega t &= \frac{2\pi}{4} = \frac{\pi}{2} \end{aligned} \right\}$$

Polarizaciones elípticas.

Sentido Horario.







